


Audio output behaves like a voltage source that droops as you draw more and more current. Output impedance, measured in ohms (Ω), characterizes the droop. More Ω more droop. Typically a BJT will require 1/100th to 1/20th the current it is driving at 0.6V, e.g. you need 1-5mA of control current at 0.6V to drive a 100mA load current. How do typical audio outputs measure up to this requirement?

Dell Laptop (200Ω, 4.6mA@0.6V)



DROK TDA7297 12V amplifier

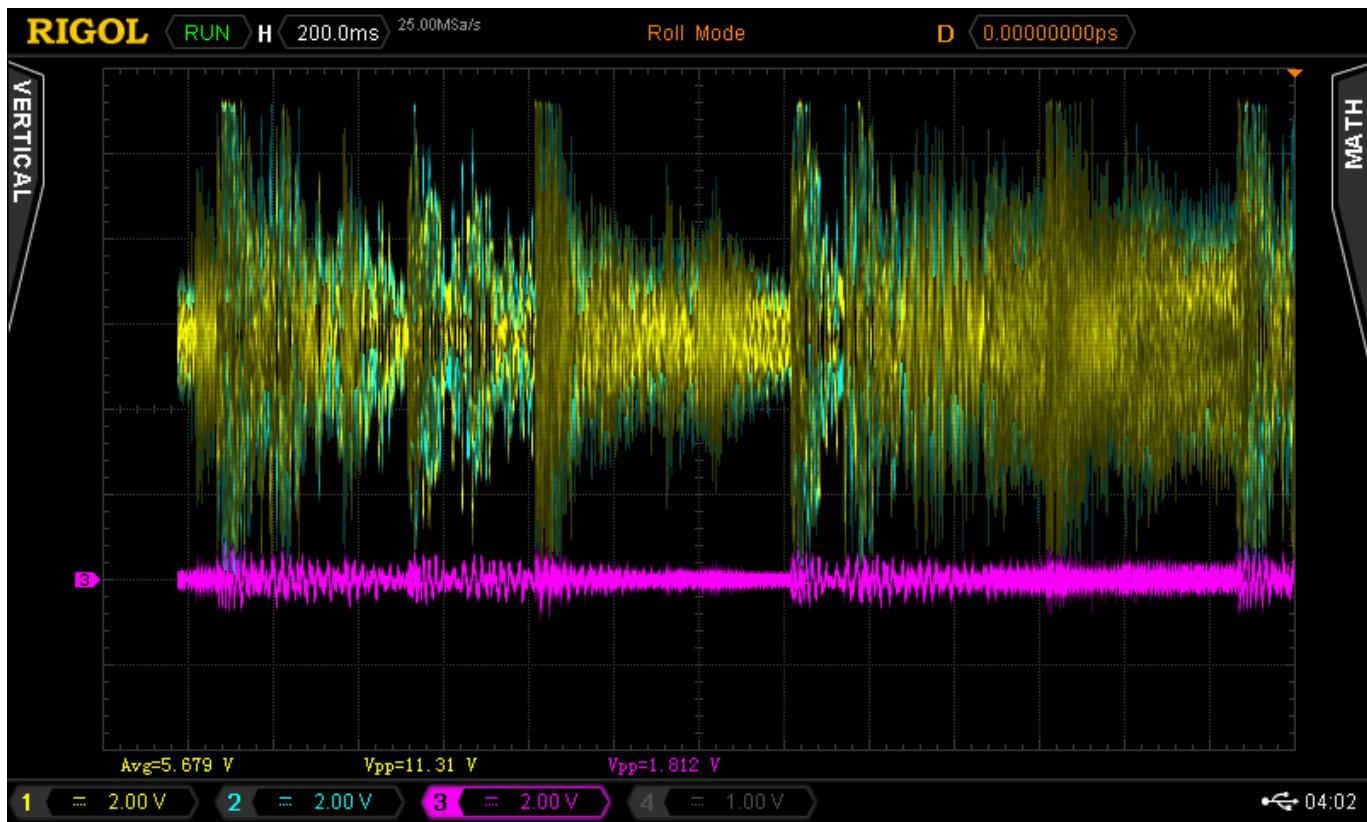We can't drive an estim circuit directly from audio output - it can barely reach 1V at max volume let alone 100V+ - but can we use audio output to drive an off-the-shelf amplifier which in turn drives an estim? True to its name, it can boost ~1V audio to 12V.



From:
<https://play-link.com/wiki/> - PlayLink

Permanent link:
https://play-link.com/wiki/doku.php?id=how_audio_output_works&rev=1467520314

Last update: **2016/07/03 04:31**